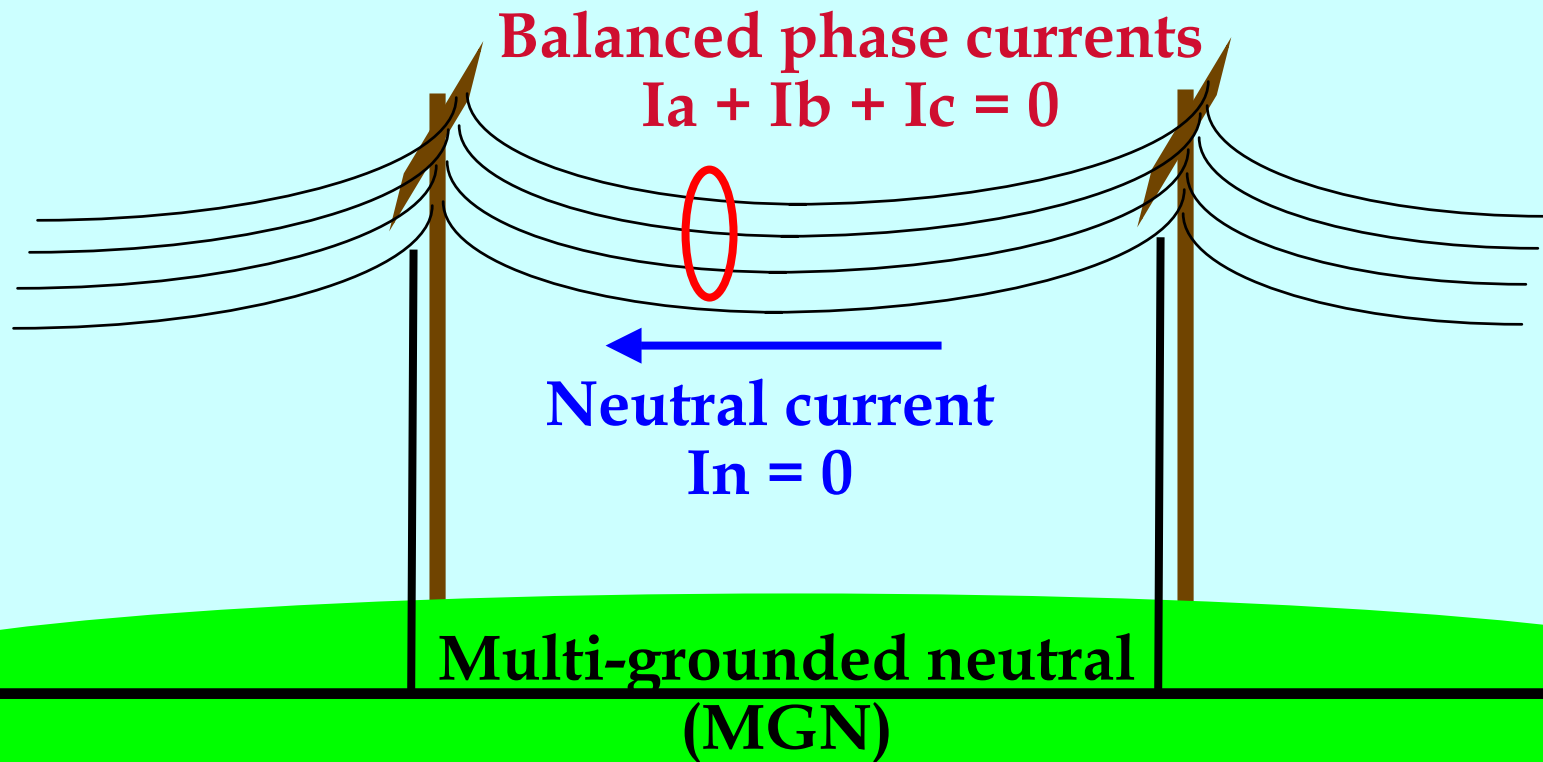


# *Distribution Harmonic Issues: Telephone Noise*

Ward Jewell  
Wichita State University


© 2002 Wichita State University

# Balanced system, no harmonics


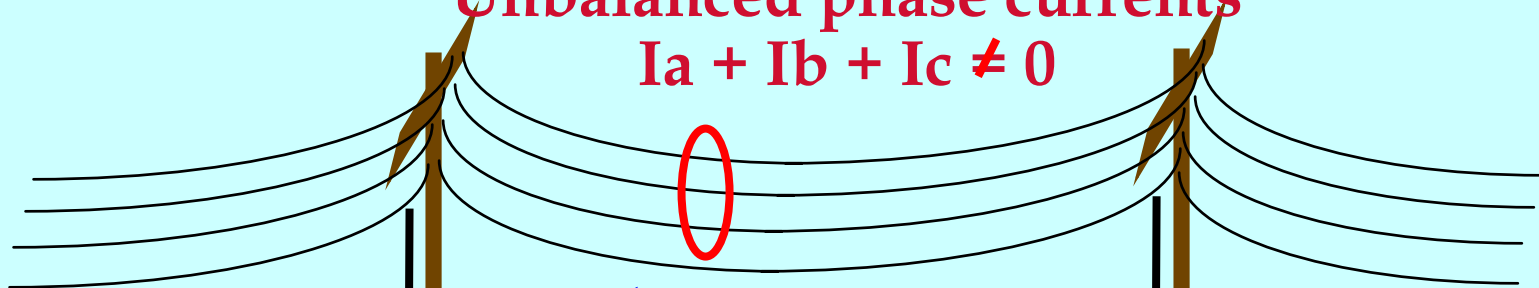
# Unbalanced system, no harmonics


Unbalanced phase currents  
 $I_a + I_b + I_c \neq 0$



Neutral current  
 $I_n = I_a + I_b + I_c$

Multi-grounded neutral  
(MGN)

# *Return current*

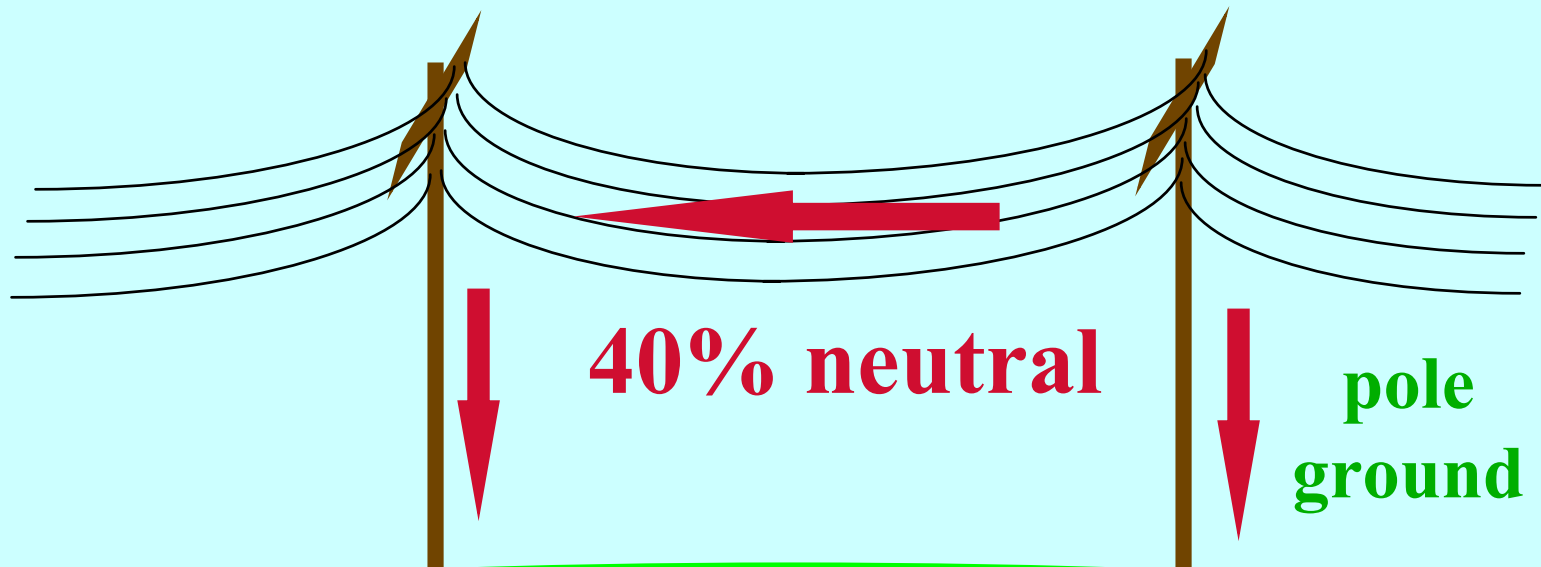


**40% neutral**

**pole  
ground**

**60% earth**

# Balanced system, harmonics

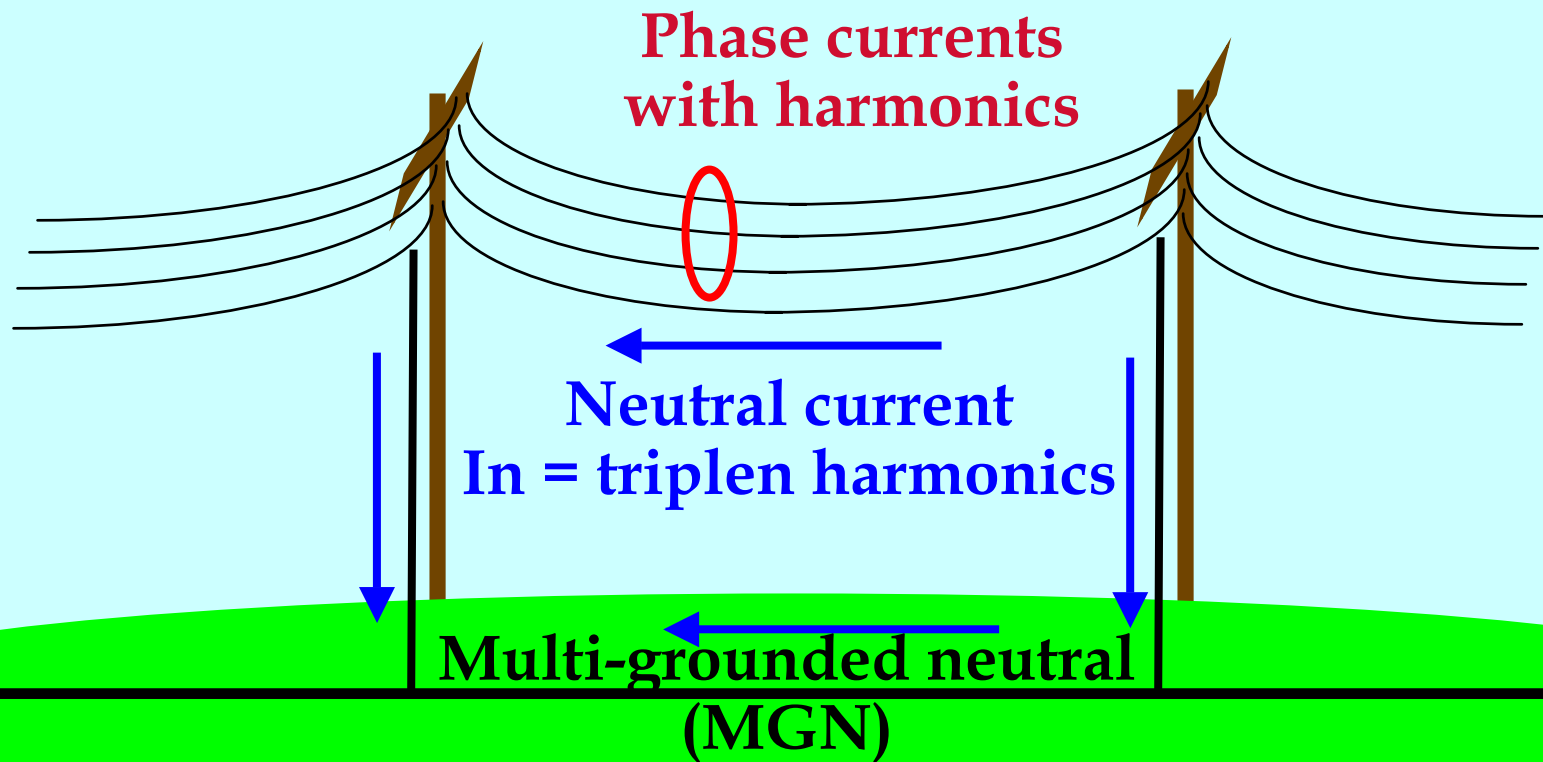


# *Neutral current flows in MGN*

increases net disturbing magnetic field


Phase currents

Neutral current

Multi-grounded neutral  
(MGN)

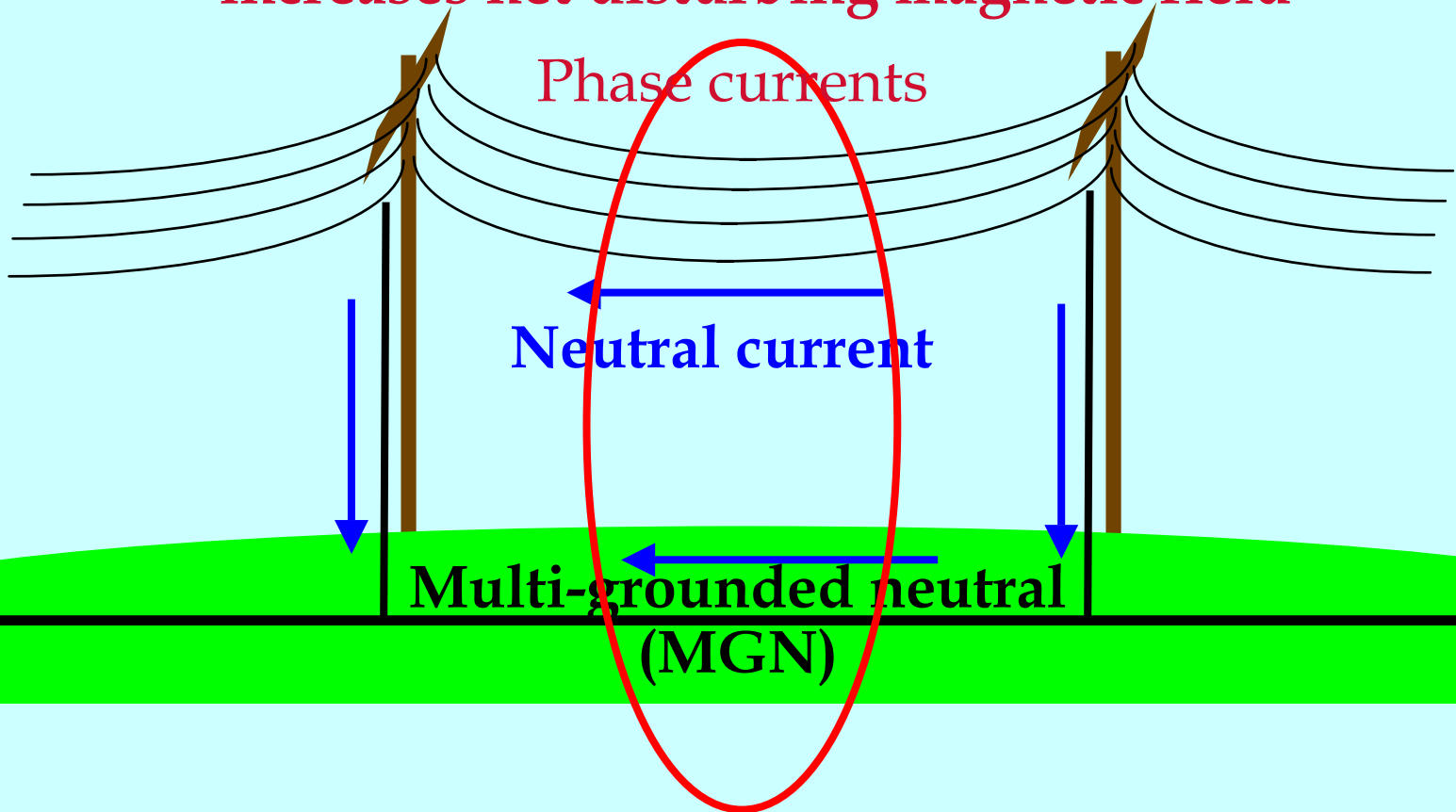

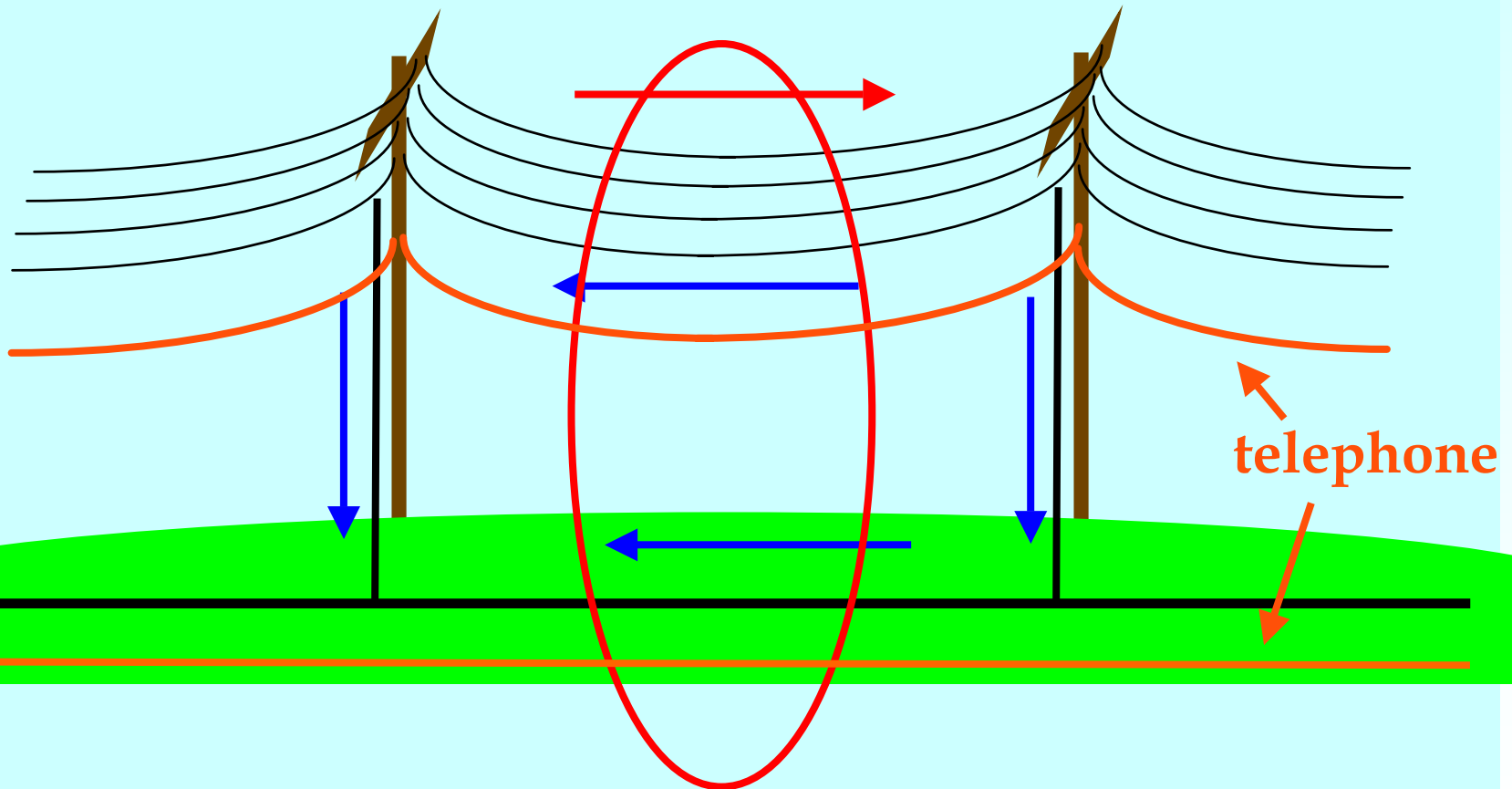
*Net disturbing field  
couples with telephone conductors,  
induces noise*



# Shielding

*Number of phase  
conductors changes*

*Feeder changes  
direction*

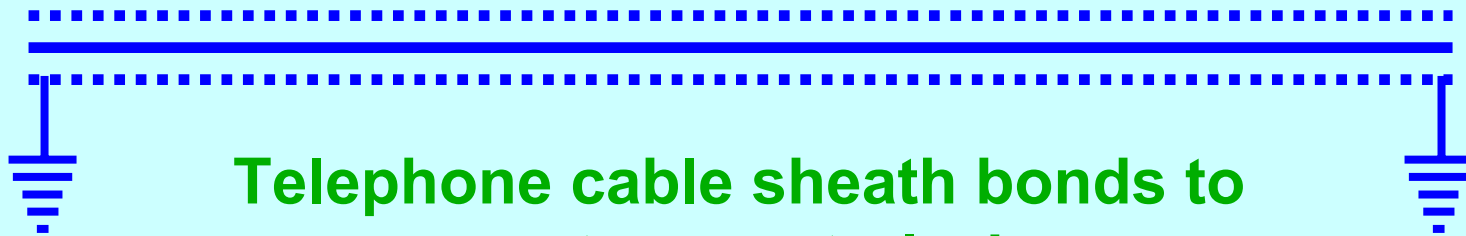


**Telephone cable sheath bonds to  
power system neutral wherever  
exposure changes.**

**Other devices and techniques help,  
but none can completely mitigate high noise levels.**




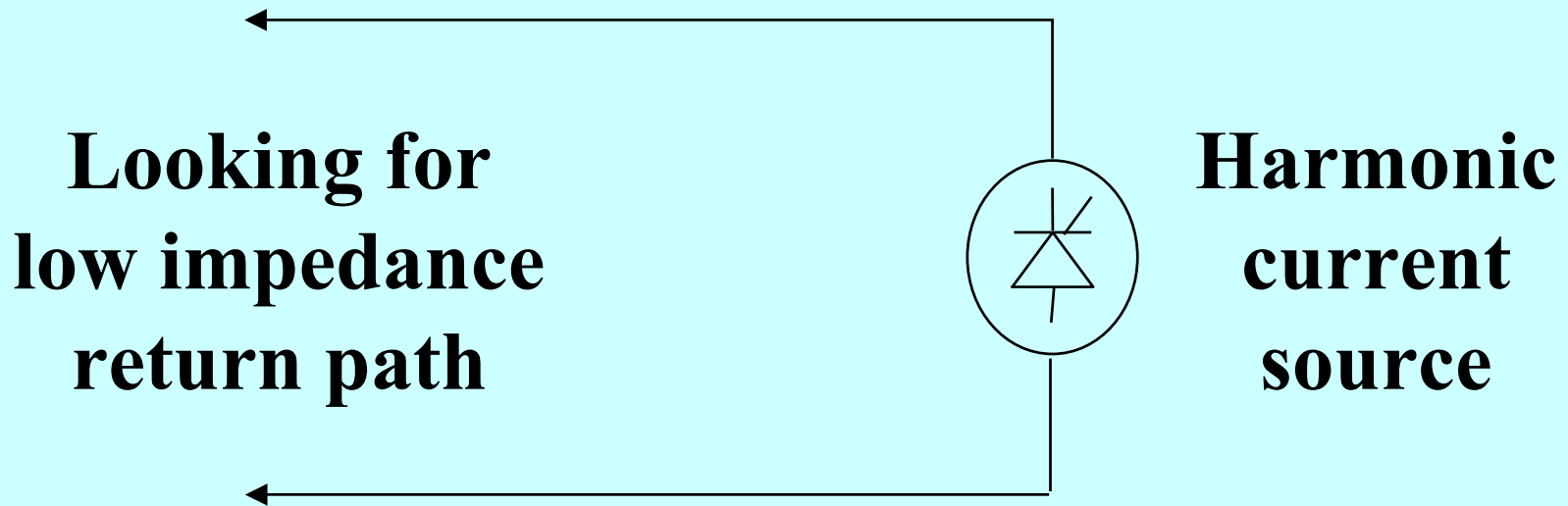*Harmonic current flows from  
and returns to its source:*


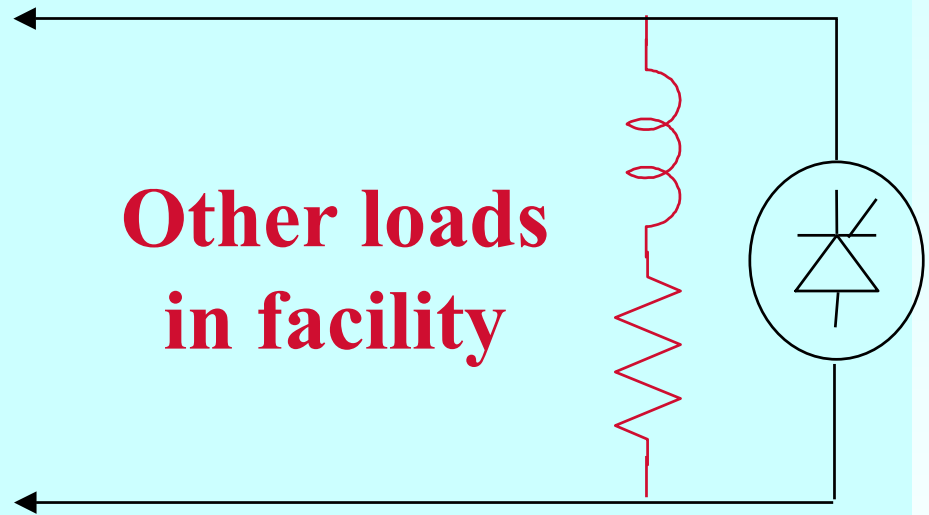
# *Harmonic return path*

**Inductive:**  
 $X = 2\pi fL$   
increases  
with frequency




**Capacitive:**

$$X = \frac{1}{2\pi fC}$$


**decreases  
with frequency**

**Low voltage  
capacitors**

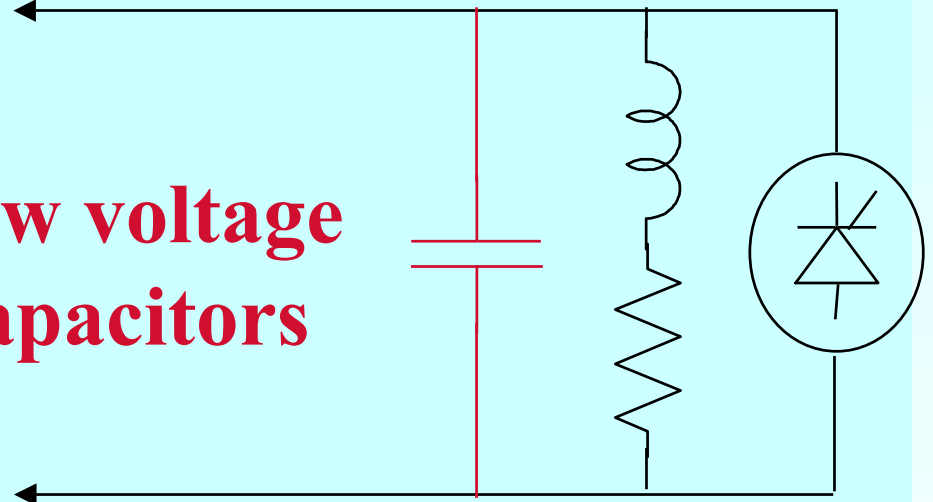

# *First ground*



**Transformer  
(high Z)**

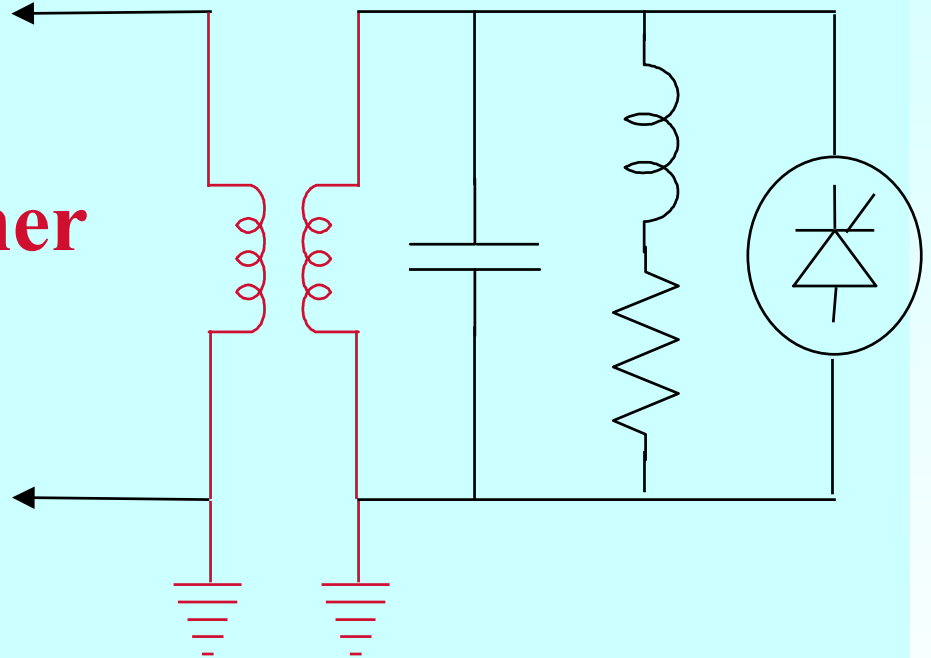

# Delta-Y transformer

*Balanced 3rd, 6th, 9th ...  
harmonics circulate  
in delta winding*




**Reduced  
triplen  
harmonics**

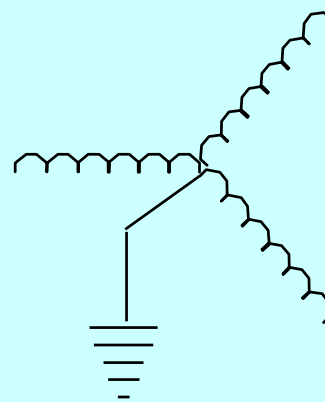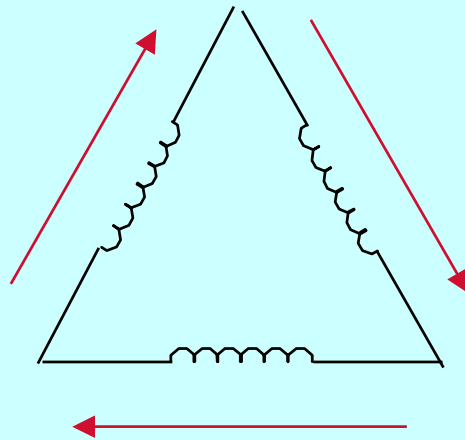




**Harmonic  
source**




# *Delta - Y transformer*

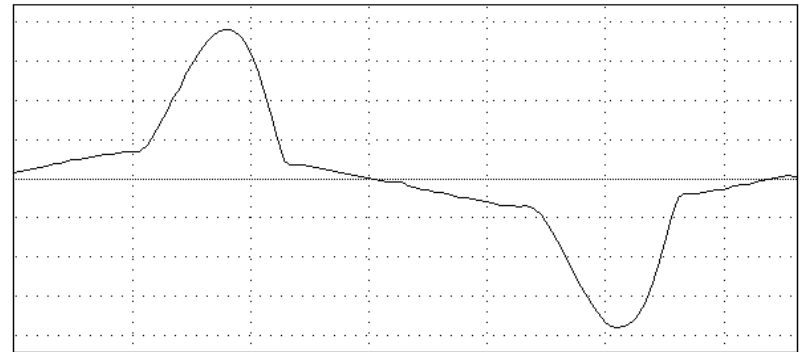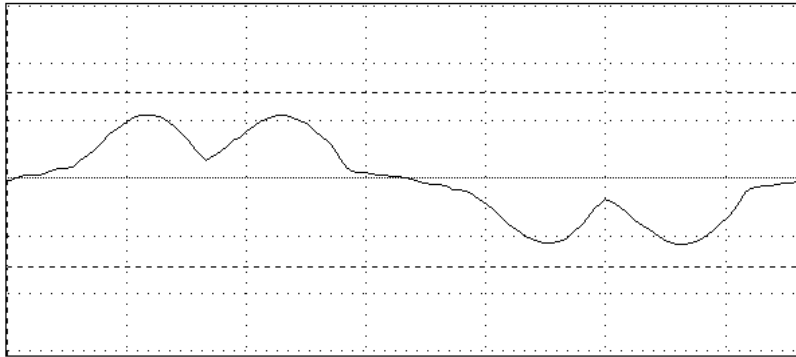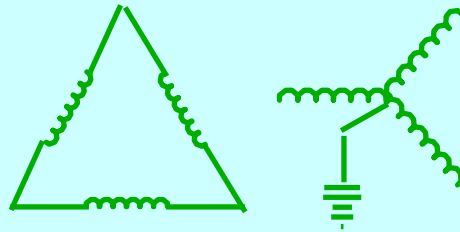

# Delta - Y transformer

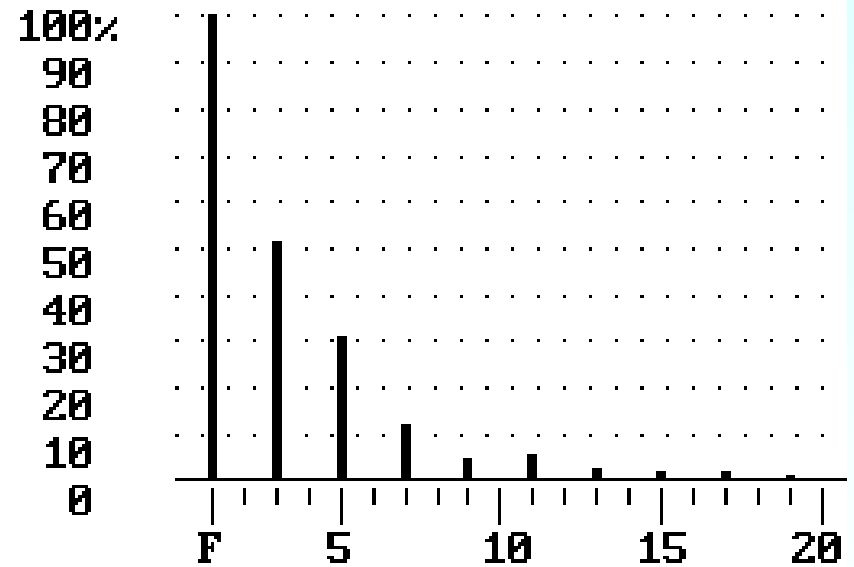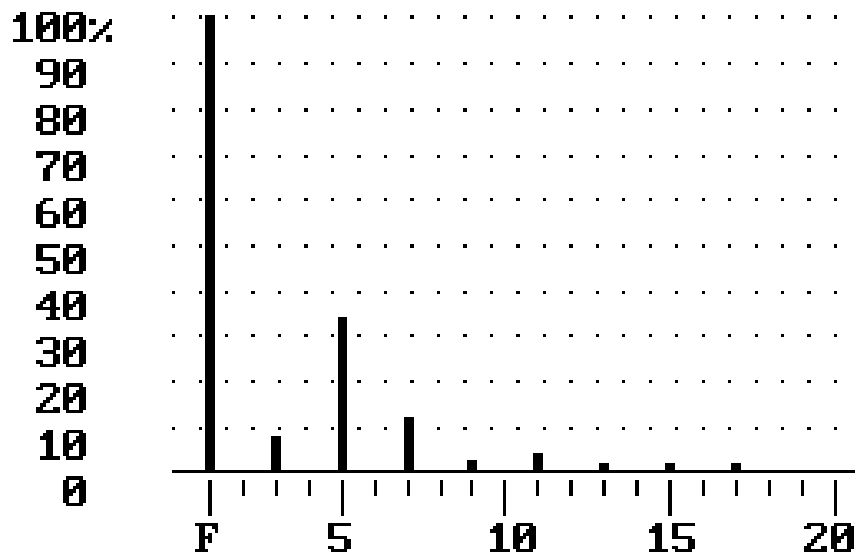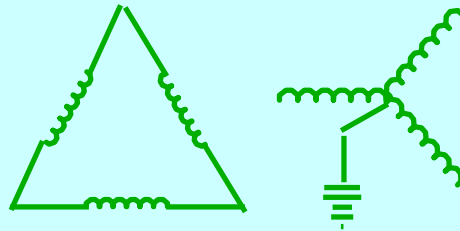


**Other  
customers'  
loads**

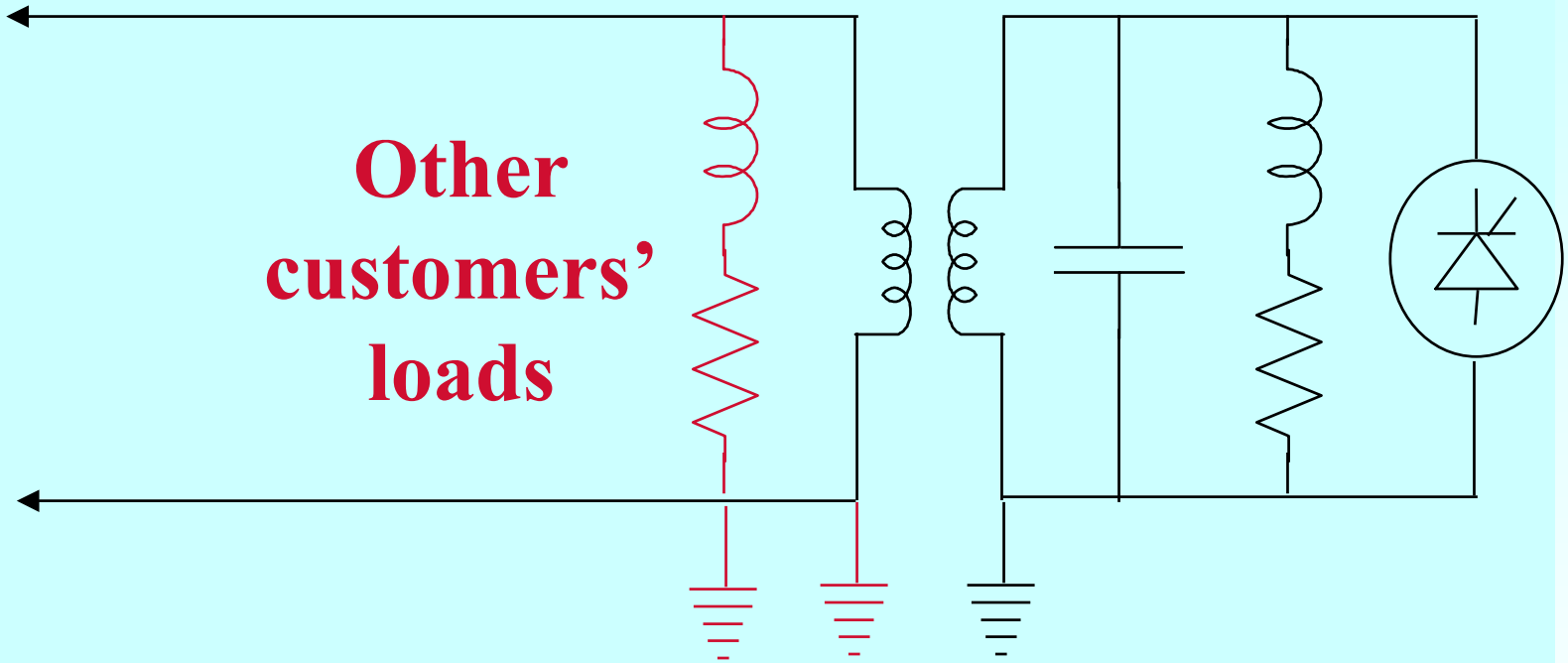

**Earth  
current**




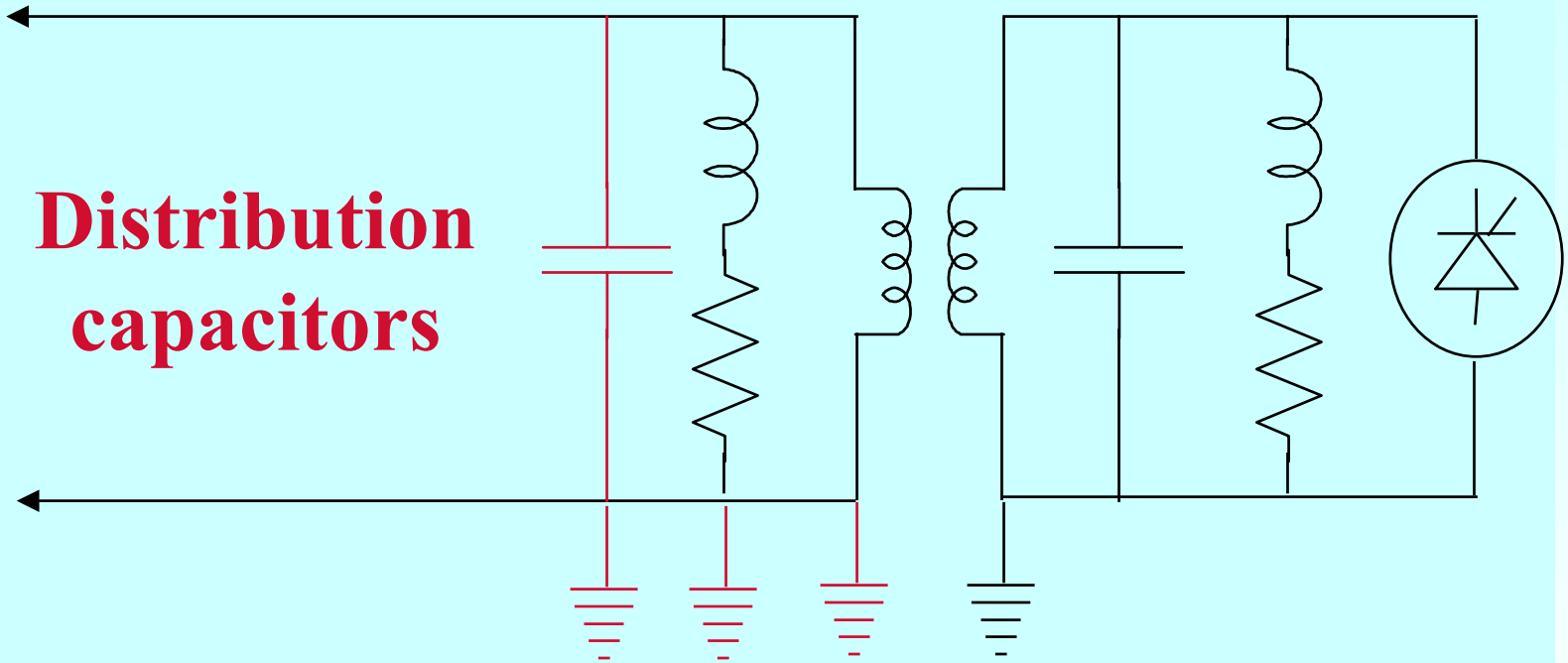


**Distribution capacitors**

**Earth current**

# *Triplen harmonics (3, 6, 9, 12 ...) flow in neutral and earth*

**All  
harmonics**

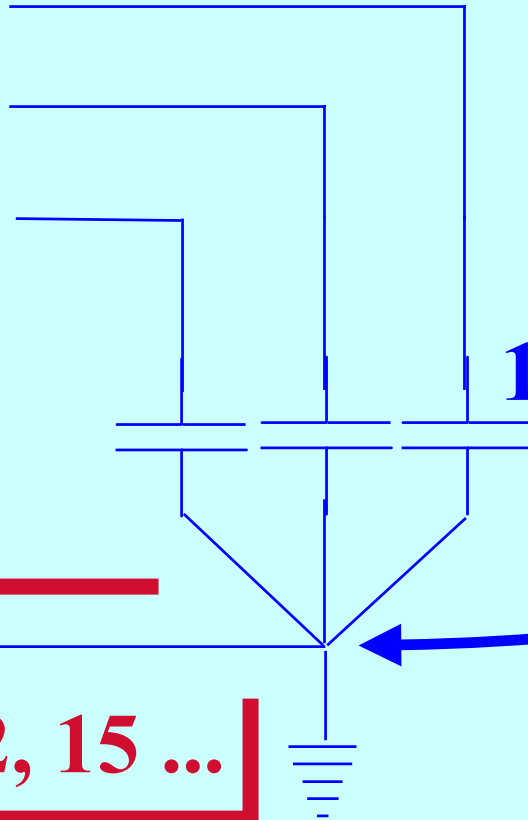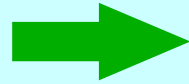


**balanced**

**1, 2 \_ 4, 5 \_ 7, 8 ...**

**sum to zero**

**3, 6, 9, 12, 15 ...**



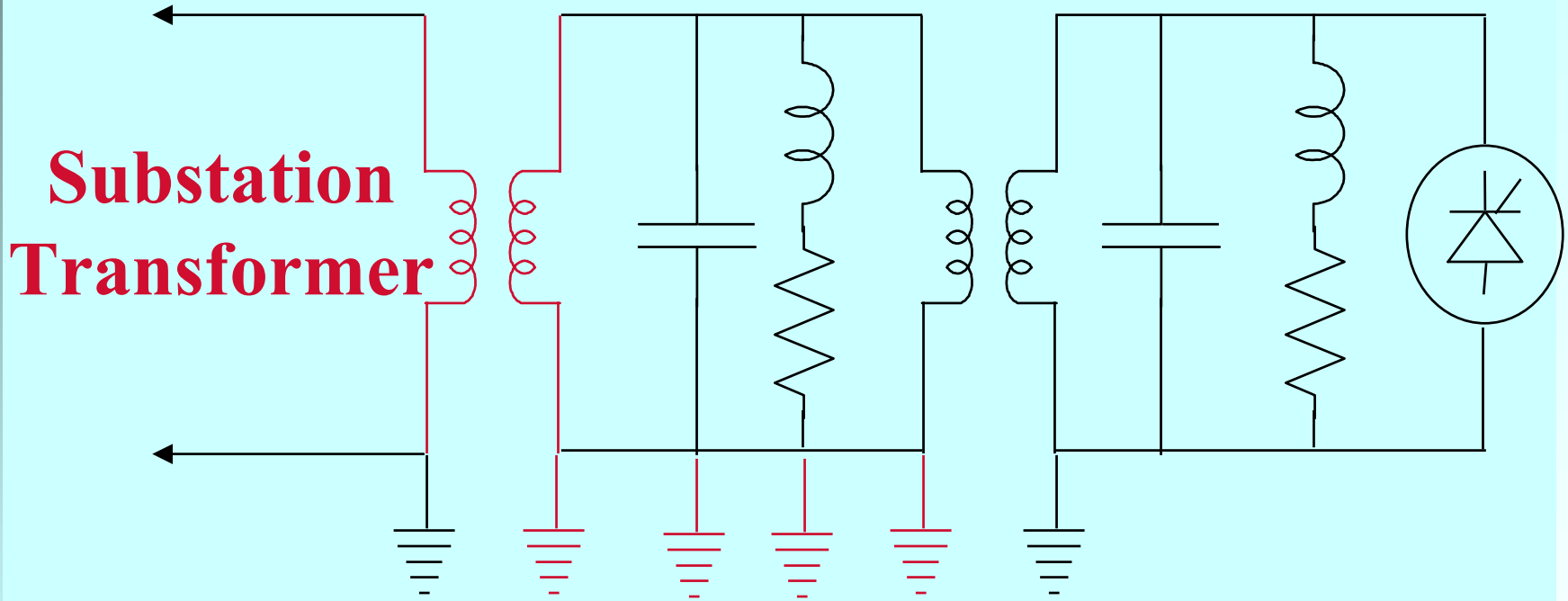


**Substation  
Transformer**

**Earth  
current**




# *Case Study*

# *Exposure to power distribution*

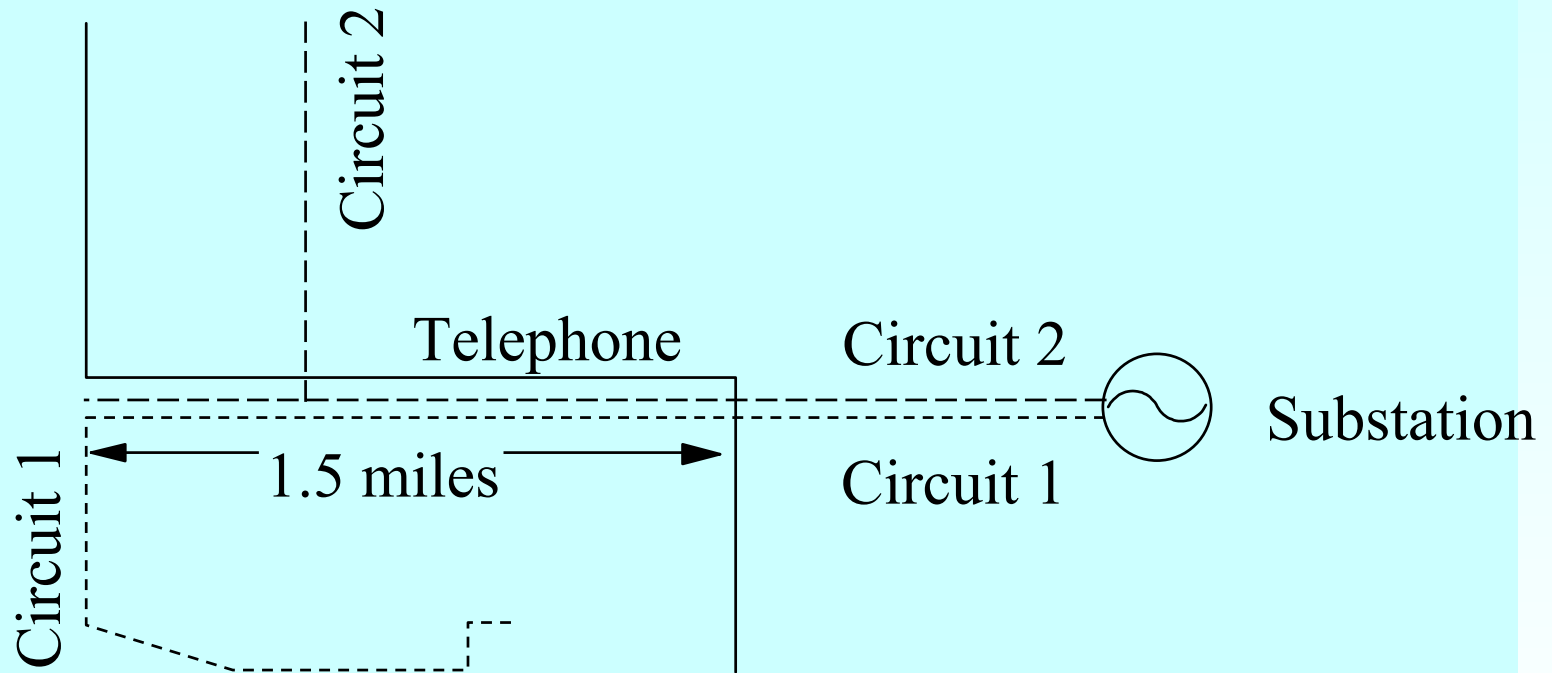

# Capacitor Resonance

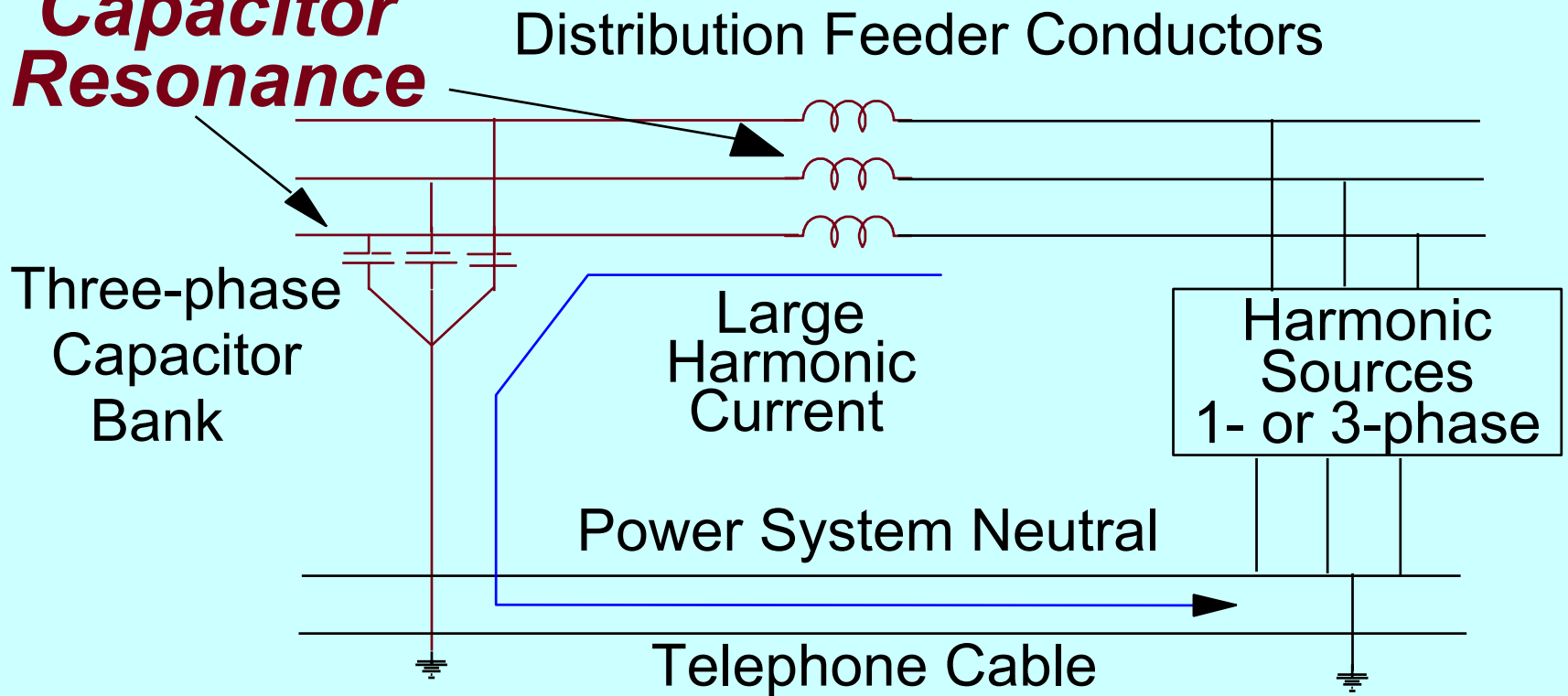

## Characteristics:

Higher harmonic current at one frequency


Change in harmonic current at capacitor bank

Significant change in harmonic current when bank switches off




# Capacitors: parallel resonance

$$LC = \frac{1}{2\pi f}$$

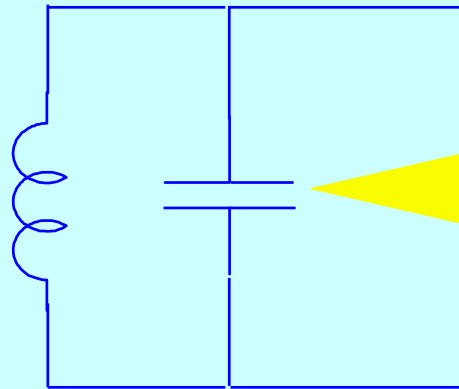


**Very high  
impedance  
at frequency “f”**

# Capacitors: parallel resonance

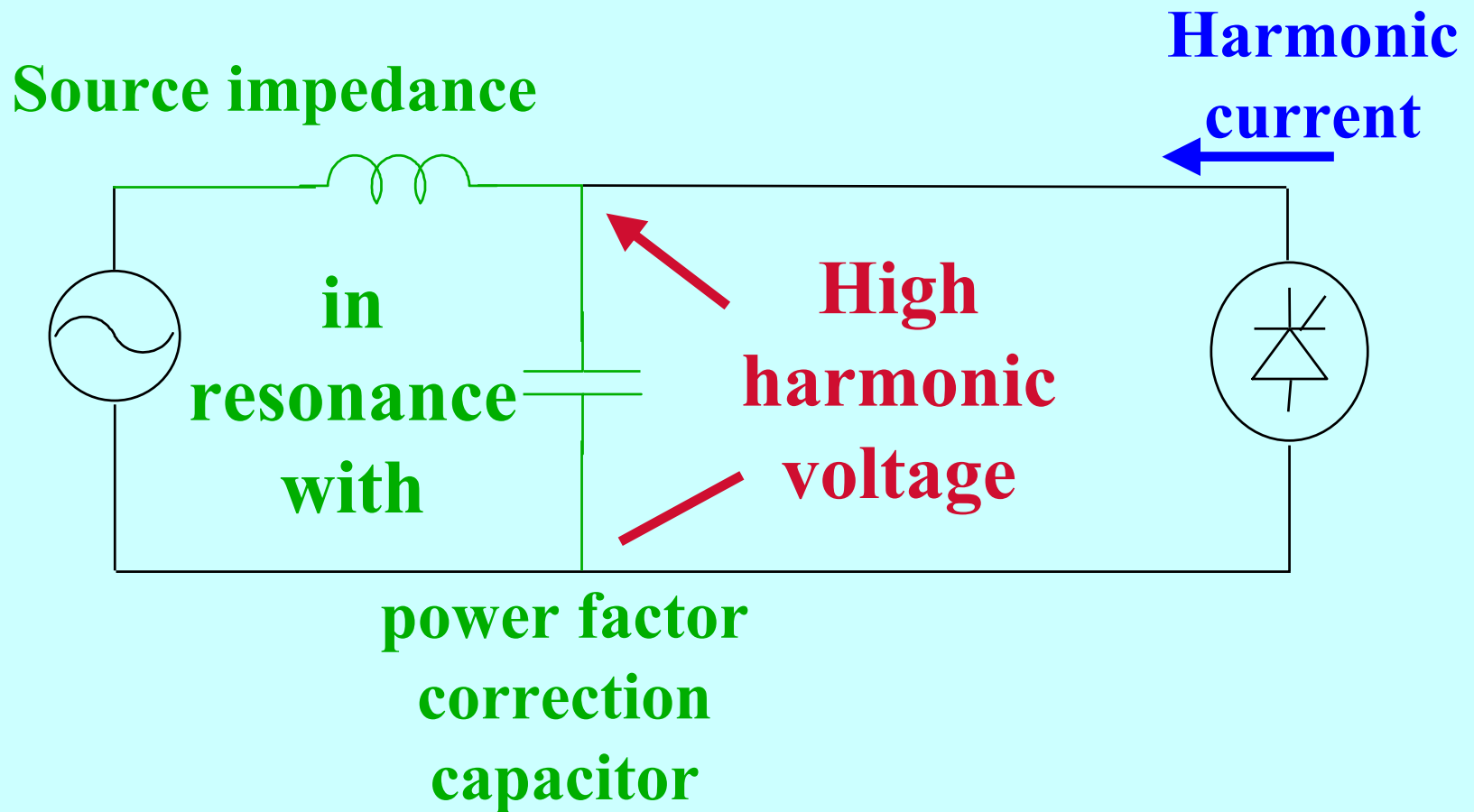
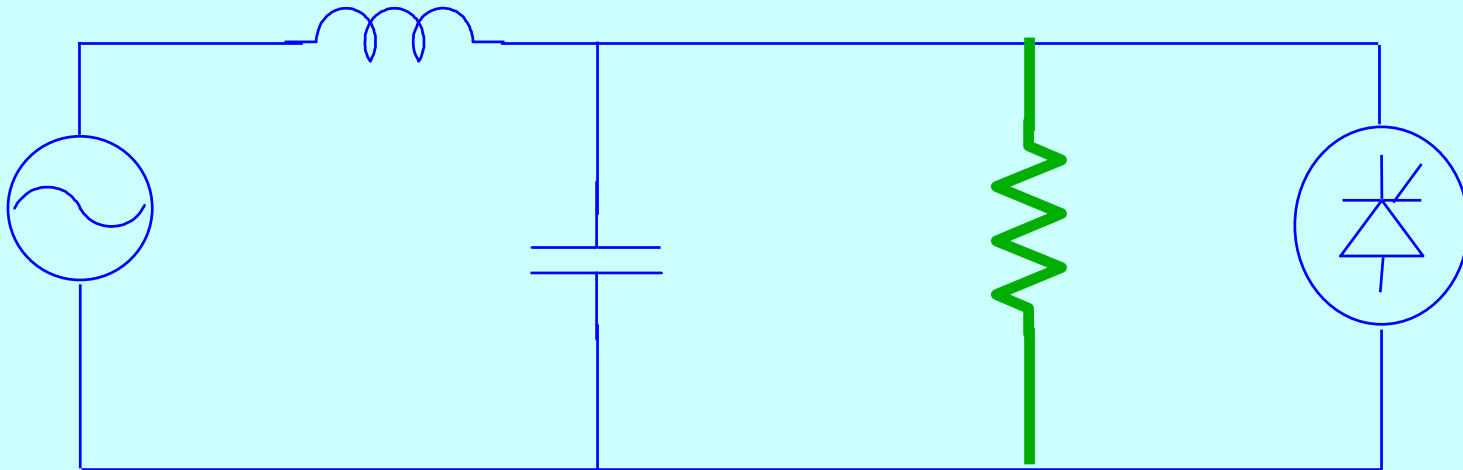
# *Parallel resonance worse with light loads*




**Load damps resonance**



# Capacitors: series resonance

$$LC = \frac{1}{2\pi f}$$

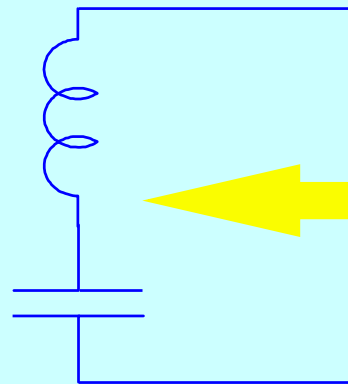

**Very low  
impedance  
at frequency “f”**



# Capacitors: series resonance

**Line reactance**

**in**

**resonance**

**with**


**power  
factor  
correction  
capacitor**



**High harmonic  
current**


**power  
factor  
correction  
capacitor**
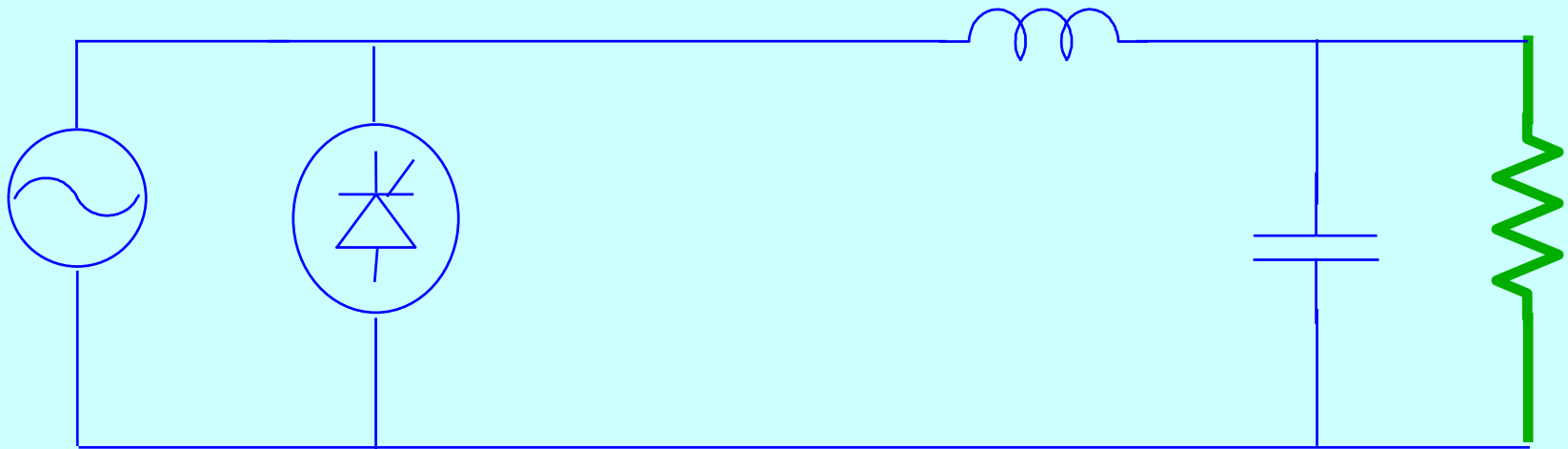
# *Series resonance worse with light loads*




**Load damps  
resonance**



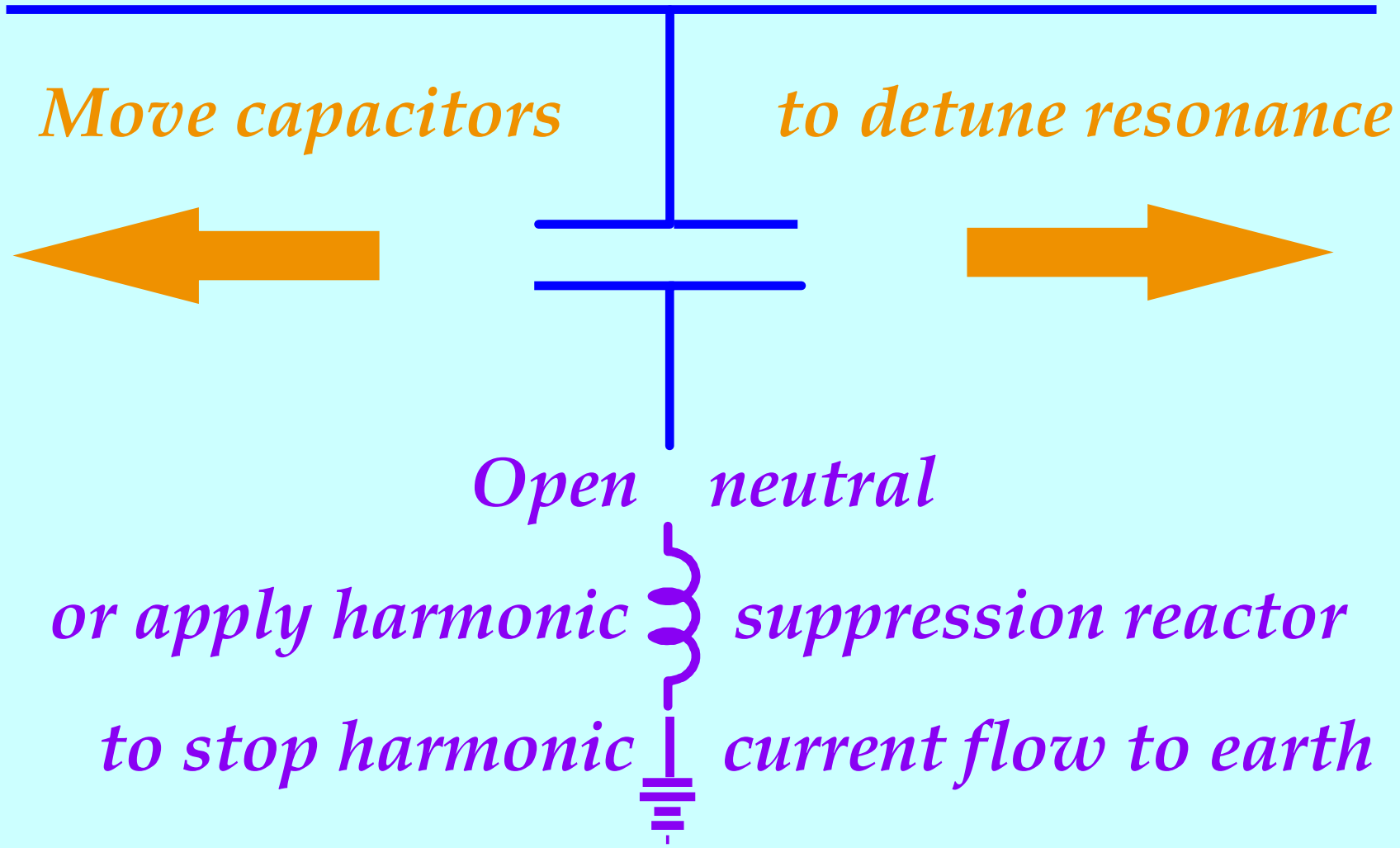

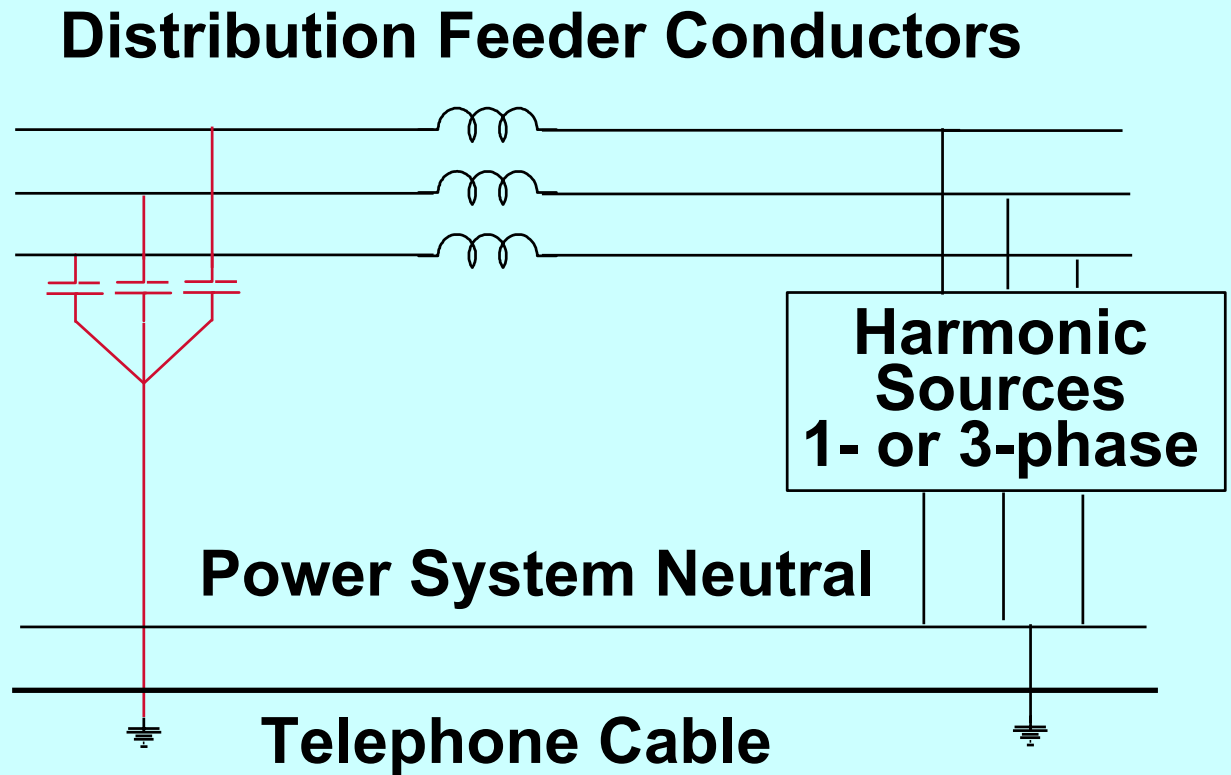
# OPEN CAPACITOR FUSES


*Open fuses on one or two capacitors causes large neutral/earth current*



# ***LARGE HARMONIC SOURCE***

**Distribution Feeder Conductors**

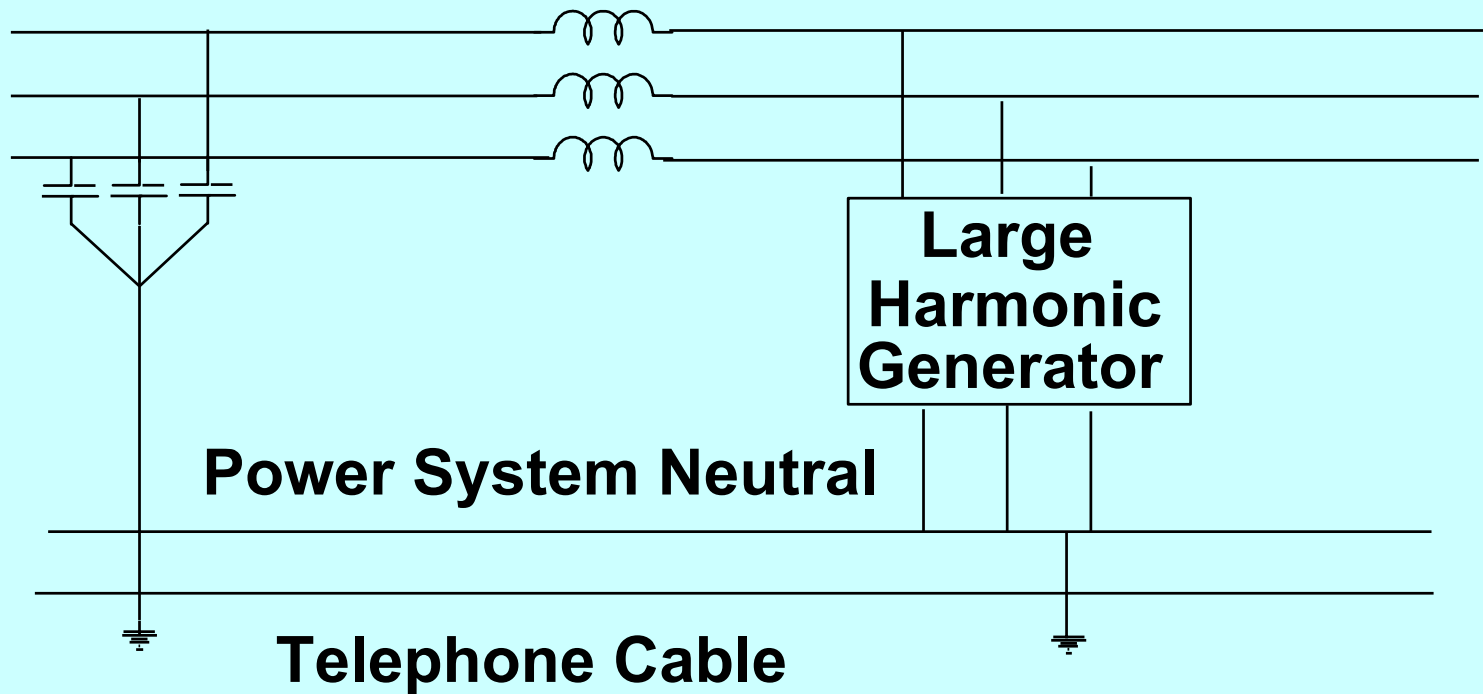


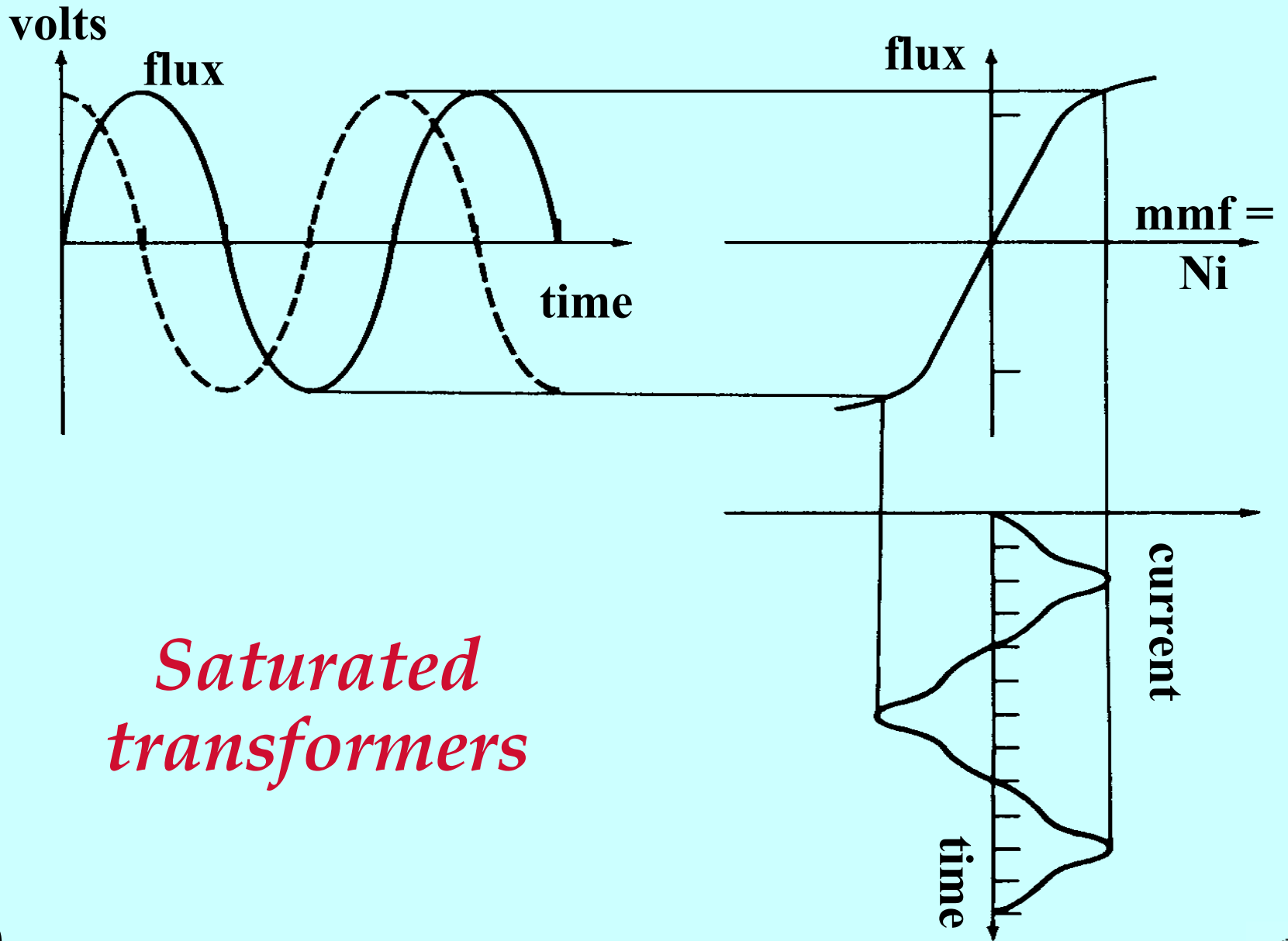

*Saturated transformers*




## Distribution Feeder Conductors

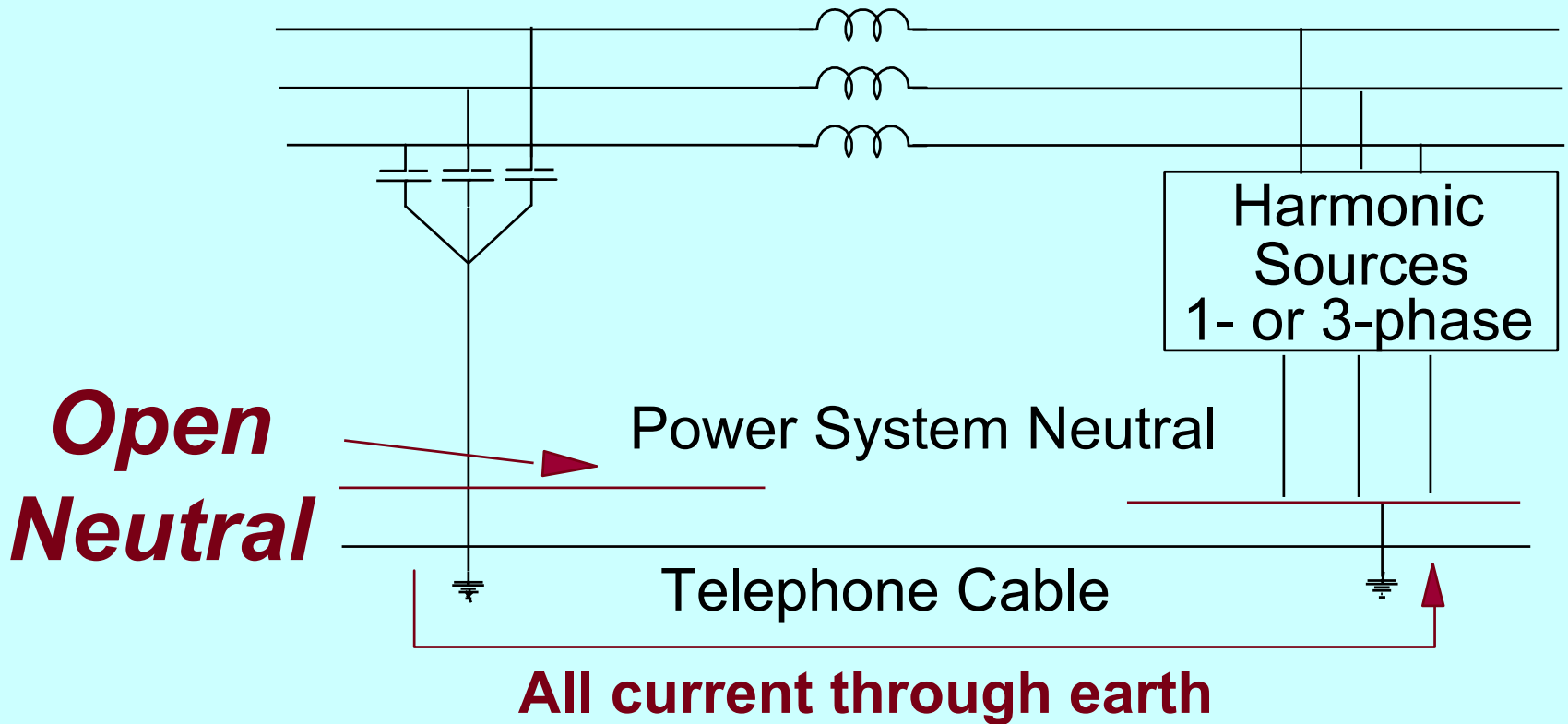


### Characteristics:

**Significant increase in noise  
between two earth connections**


# *Small harmonic sources*

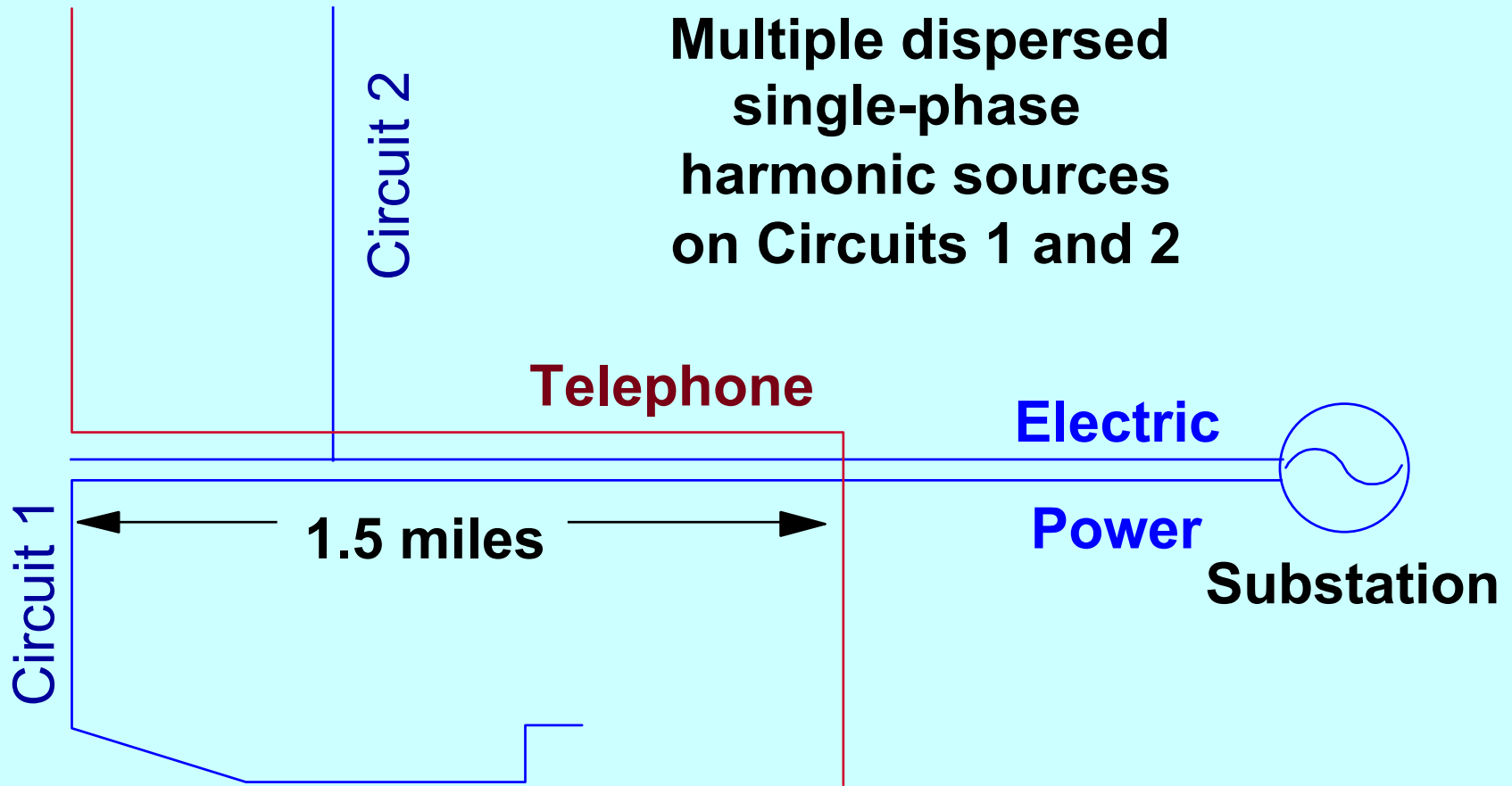


# *Model the system*

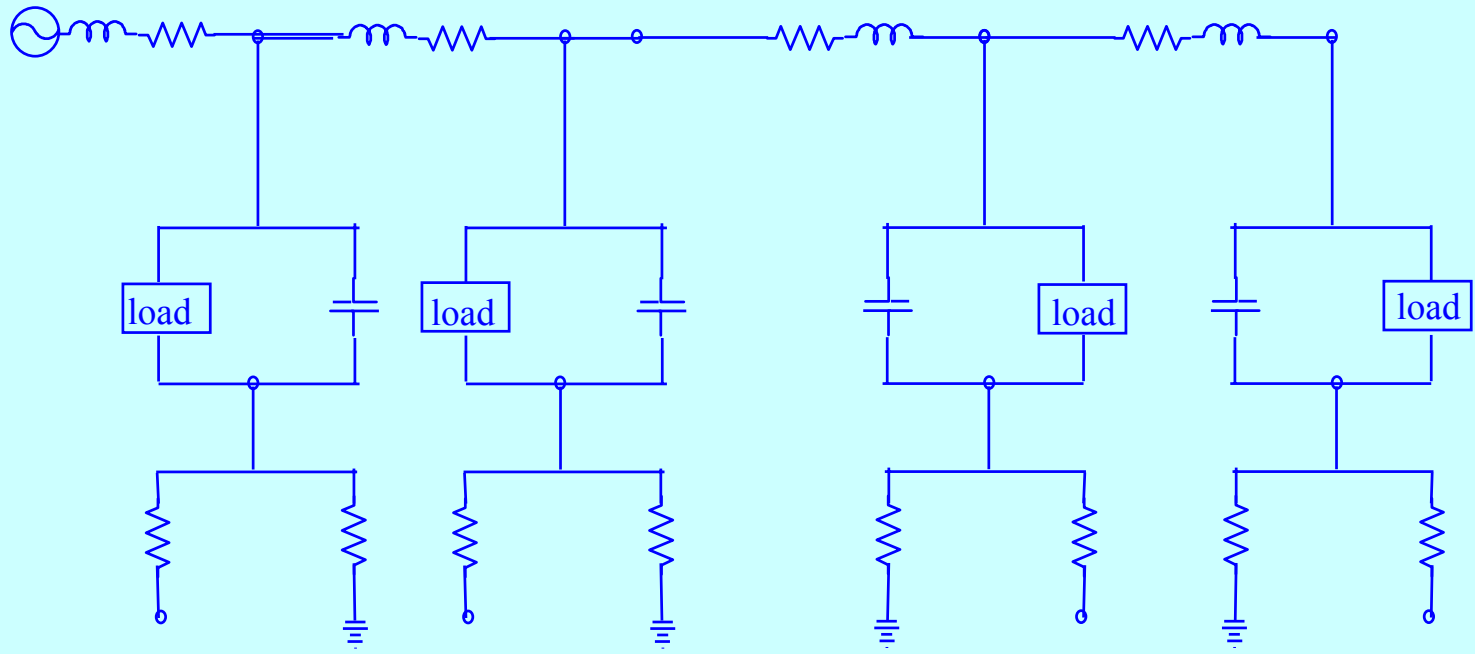

# ***SMALL HARMONIC SOURCES: SOLUTION***

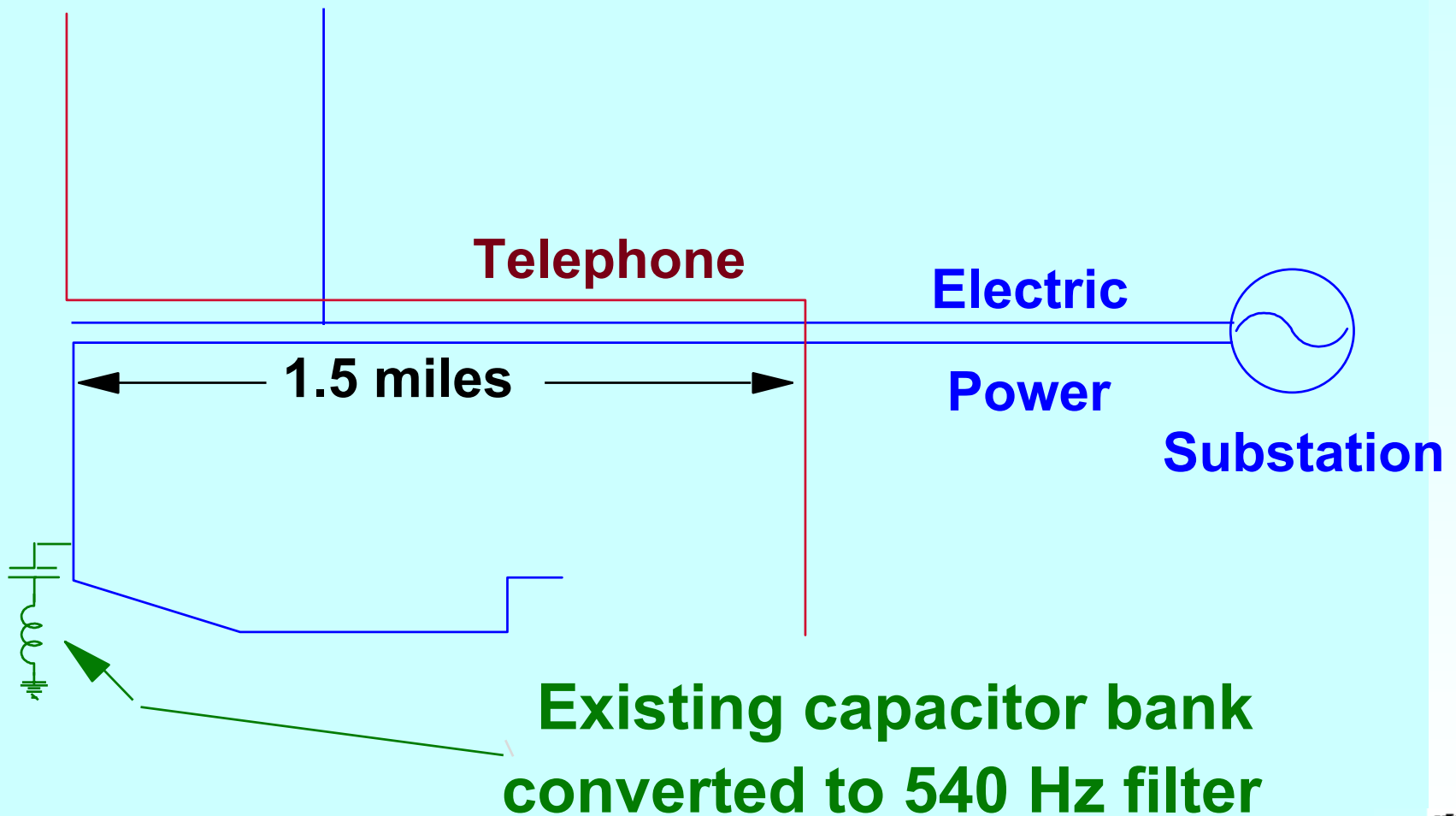

# *Convert capacitor to shunt filter*

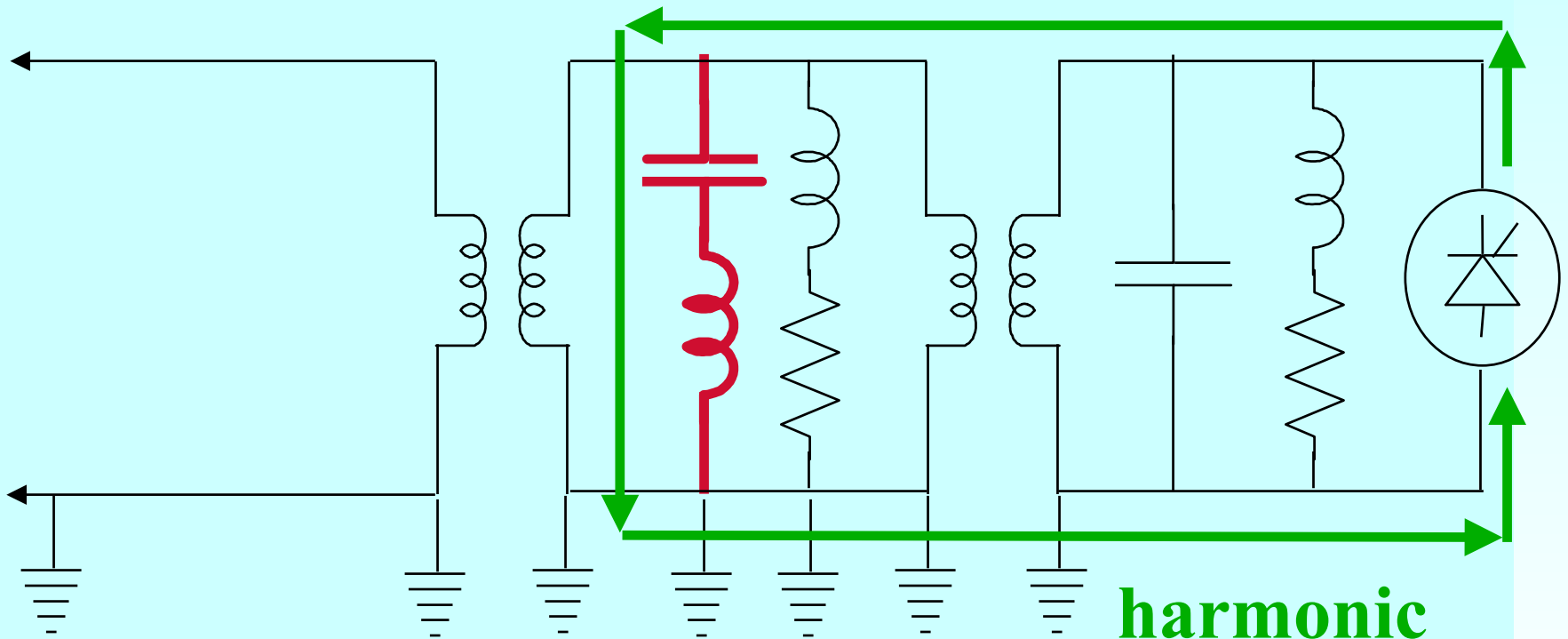

**earth current is reduced**

**harmonic  
current  
returns**



# *Shunt harmonic filter*

Filter frequency:  $2 \cdot \pi \cdot f := \frac{1}{\sqrt{L \cdot C}}$

**Example:**


**$f = 540$  Hz (9th harmonic of 60 Hz)**

**C is 7200 V, 600 kVAR bank:  $C = 10.2 \mu\text{F}$**

**$L = 8.5$  mH**



# Harmonic filter

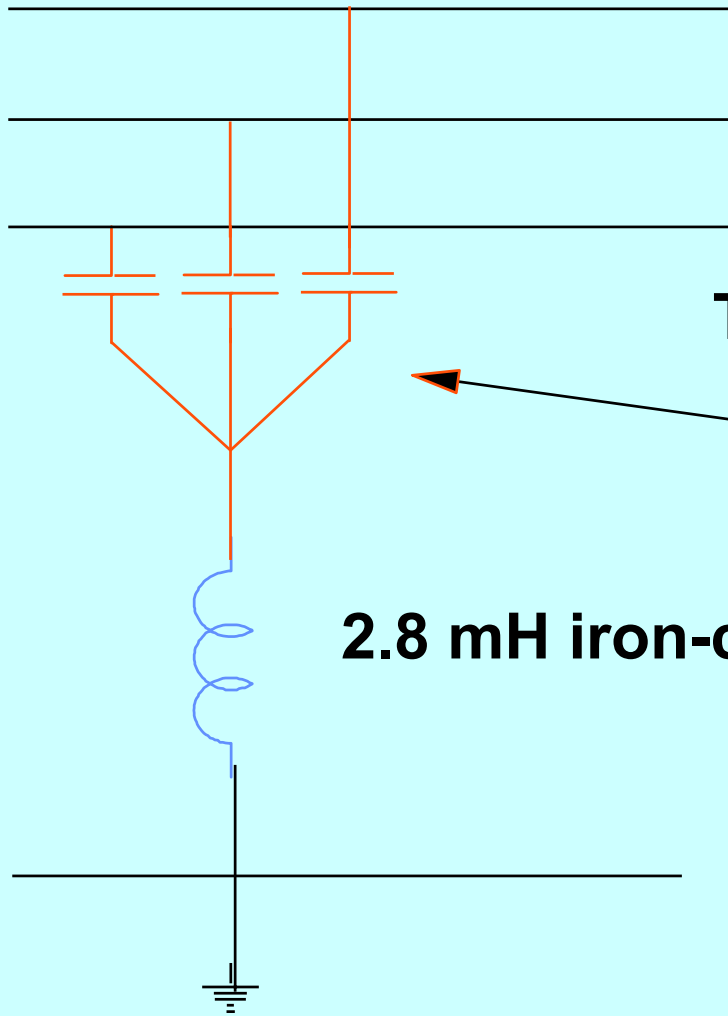

Three-phase capacitor bank

2.8 mH iron-core inductor

# *Telephone noise causes/solutions*

- Capacitor resonance
  - Move capacitor
  - Open capacitor neutral
  - Harmonic suppression reactor
- Open capacitor fuse
  - Replace fuse
- Large harmonic source
  - Mitigate at source
- Saturated transformer
  - Repair or replace transformer
  - Reduce feeder voltage
- Small distributed harmonic sources
  - Reconfigure feeder
  - Upgrade phone to fiber
  - Filter

# *Questions or Comments?*

Contact Ward Jewell at (316) 978-6340 or  
[ward.jewell@wichita.edu](mailto:ward.jewell@wichita.edu)

Further reading:

Ward Jewell, Bill Miller, Tom Casey, "Filtering Dispersed Harmonic Sources on Distribution," *IEEE Transactions on Power Delivery*, Vol. 15, No. 3, July 2000, pp. 1045-1051.